

Practical 5: To Realize Half Adder, Full Adder, Half Subtractor & Full Subtractor Using Basic Gates and NAND Gates

Adders and subtractors are digital circuits used for arithmetic operations in computers.

They are built using logic gates like **AND, OR, XOR, NOT, NAND** etc.

In this practical, we study:

- Half Adder
- Full Adder
- Half Subtractor
- Full Subtractor

And how to implement them using **basic gates** and **NAND gates** (**universal gate**).

HALF ADDER

Function:

Adds two single-bit binary numbers.

Inputs: A, B

Outputs:

- $\text{SUM} = A \oplus B$
- $\text{CARRY} = A \cdot B$

(A) Realization Using Basic Gates

- SUM \rightarrow XOR Gate
- CARRY \rightarrow AND Gate

Truth Table:

A	B	SUM (A \oplus B)	CARRY (A \cdot B)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(B) Realization Using NAND Gates

We know:

- XOR can be built using 4 NAND gates
- AND = NAND followed by NOT (which is also NAND)

Thus the whole Half Adder can be made using **only NAND** gates.

FULL ADDER

Function:

Adds three bits (A, B, Carry-in).

Inputs: A, B, Cin

Outputs:

- **SUM** = $A \oplus B \oplus \text{Cin}$
- **CARRY** = $(A \cdot B) + (\text{Cin} \cdot (A \oplus B))$

(A) Realization Using Basic Gates

Uses:

- Two XOR gates \rightarrow for SUM
- Two AND gates + one OR gate \rightarrow for CARRY

Truth Table:

A	B	Cin	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(B) Realization Using NAND Gates

All basic operations (XOR, AND, OR) can be implemented using NAND gates only.

So Full Adder can be fully realized using **NAND-only circuit**.

HALF SUBTRACTOR

Function:

Subtracts two single-bit numbers: $A - B$

Inputs: A, B

Outputs:

- **DIFFERENCE** = $A \oplus B$
- **BORROW** = $\neg A \cdot B$

(A) Realization Using Basic Gates

- Difference \rightarrow XOR gate
- Borrow \rightarrow AND + NOT gate

Truth Table:

A	B	DIFFERENCE ($A \oplus B$)	BORROW ($\neg A \cdot B$)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

(B) Realization Using NAND Gates

- NOT using NAND
- AND using NAND
- XOR using NAND

Thus Half Subtractor can also be formed completely with NAND gates.

FULL SUBTRACTOR

Function:

Subtracts three bits: $A - B - \text{Borrow-in}$

Inputs: A, B, Bin

Outputs:

- **DIFFERENCE** = $A \oplus B \oplus \text{Bin}$

- **BORROW** = $(\neg A \cdot B) + (\neg(A \oplus B) \cdot \text{Bin})$

(A) Realization Using Basic Gates

Uses:

- XOR gates
- AND gates
- OR gates

Truth Table:

A	B	Bin	DIFFERENCE	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0

1	1	0	0	0
1	1	1	1	1

(B) Realization Using NAND Gates

As NAND gates can create all basic operations, the full subtractor can also be built using only NAND gates.